

DDCO

UNIT-1

CLASS NOTES

feedback/corrections: vibha@pesu.pes.edu

Vibha Masti 

introduction

Course instructor: Dr. Reetinder Sidhu, reetindersidhu@pes.edu

- knowledge of hardware essential for efficient software


Moore's Law

- ~30 years ago, supercomputers needed liquid nitrogen
- Every ~18 months, no. of transistors per chip area doubles
- Transistor speed 2x, power consumption $\frac{1}{2}$ x.
- Moore's Law is now slowing down
- Therefore, to improve performance, deeper knowledge of hardware needed for good software
- Targeted hardware accelerators developed
- Google has TensorFlow & Tensor Processing Unit accelerators

BOOLEAN FUNCTIONS

Mathematical Functions

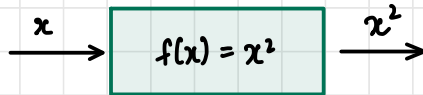- Example: parabola
- Domain & range set of real numbers
- Can be specified on Cartesian plane
- Specify function as a box




Boolean Functions

- Example: AND function/gate
- Domain & range: $\{0,1\}$
- Specify function using truth table

| a | b | y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |


- Specify as logic gate (black box)

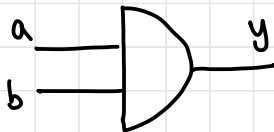



TODO: redraw


BASIC FUNCTIONS / LOGIC GATES


1) BUFFER  $y = a$

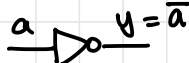2) NOT  $y = \bar{a}$

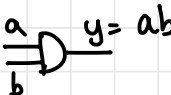
3) AND  $y = ab$

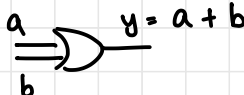4) OR  $y = a + b$

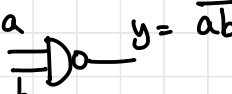5) NAND  $y = \overline{ab}$

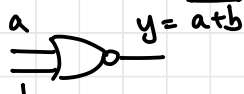6) NOR  $y = \overline{a+b}$

7) XOR  $y = a \oplus b$

8) XNOR  $y = \overline{a \oplus b}$

- Number of rows for a n -input TT = 2^n
- How many different 1-input boolean functions can exist? (2^1)

Layers of Abstraction

- Logic minimisation: truth table
- Logic design level: component in logic circuit
- CMOS VLSI design: transistor level circuit diagram with digital switches (on or off)
- VLSI layout level (silicon, metal)
- VLSI fabrication level - chip (microprocessor)

Boolean Algebra & Identities

Logic circuits

- Multiple logic gates
- O/P of one gate connected to I/P of another
- Represent Boolean functions
- Look at Perfect Induction

Boolean Formulas

- Boolean constants (0 and 1) are Boolean formulas
- Boolean variables (like x) are Boolean formulas
- If P & Q are Boolean formulas,

Precedence

| | |
|----------------|--------------------|
| 1. \bar{P} | } Boolean formulas |
| 2. $P \cdot Q$ | |
| 3. $P + Q$ | |


Q: How is $(a \cdot \bar{c}) + (b \cdot c)$ a Boolean formula?

1. a, b & c are Boolean formulas
2. \bar{c} is a Boolean formula
3. $a \cdot \bar{c}$ and $b \cdot c$ are Boolean formulas
4. $a \cdot \bar{c} + b \cdot c$ is a Boolean formula

Boolean Formulas & Logic Circuits

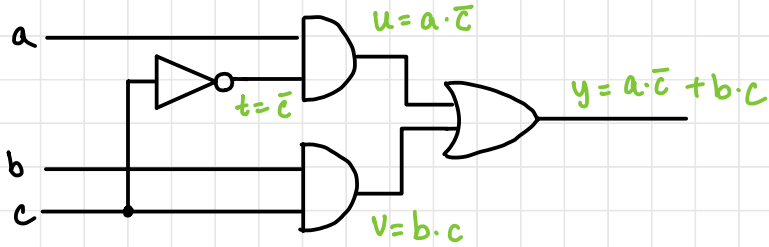1. Constants & variables are inputs to logic gates
2. \cdot operator means AND
3. $+$ operator means OR
4. $\bar{\quad}$ operator means NOT

Q: Convert $((a \cdot \bar{c}) + (b \cdot c))$ to a logic circuit



COMBINATIONAL LOGIC CIRCUITS

- Circuits that can be represented by Boolean formulas
- Unlike sequential logic circuits (with feedback)


* HDL (hardware descriptive language) not in this course.

BOOLEAN ALGEBRA & IDENTITIES

- Boolean functions can be represented as truth tables, combinational logic circuits and Boolean formulas
- Multiple Boolean functions & CLCs for Boolean formula

Note-Bubbles

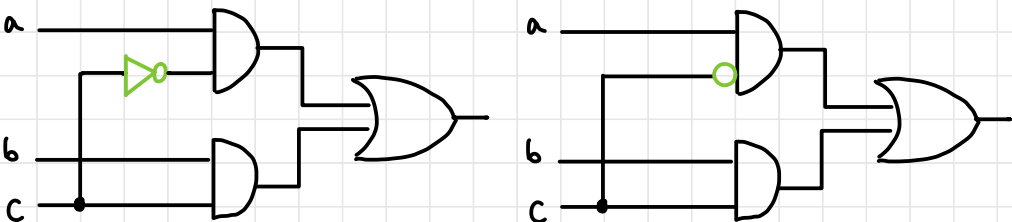- NOT gates can be replaced with a bubble



Boolean Algebra

1. Set: $\{0, 1\}$
2. Operations: AND, OR, NOT
3. Identity element: (0 - OR, 1 - AND)
4. Laws: commutative, associative, distributive

Boolean Identities

1. Commutative

$$\begin{aligned} a \cdot b &= b \cdot a \\ a + b &= b + a \end{aligned} \quad \begin{array}{l} \curvearrowright \\ \curvearrowright \end{array} \text{ dual}$$

2. Associative

$$\begin{aligned} (a \cdot b) \cdot c &= a \cdot (b \cdot c) \\ (a + b) + c &= a + (b + c) \end{aligned} \quad \begin{array}{l} \curvearrowright \\ \curvearrowright \end{array} \text{ dual}$$

3. Distributive

$$\begin{aligned} a \cdot (b + c) &= a \cdot b + a \cdot c \\ a + (b \cdot c) &= (a + b) \cdot (a + c) \end{aligned} \quad \begin{array}{l} \curvearrowright \\ \curvearrowright \end{array} \text{ dual}$$

4. De Morgan's

$$\begin{aligned} \overline{(a + b)} &= \bar{a} \cdot \bar{b} \\ \overline{(a \cdot b)} &= \bar{a} + \bar{b} \end{aligned} \quad \begin{array}{l} \curvearrowright \\ \curvearrowright \end{array} \text{ dual}$$

5. Idempotency

$$\begin{aligned} a \cdot a &= a \\ a + a &= a \end{aligned}$$

6. Identity

$$a \cdot 1 = a$$

$$a + 0 = a$$

7. Boundedness

$$a \cdot 0 = 0$$

$$a + 1 = 1$$

8. Complement

$$a \cdot \bar{a} = 0$$

$$a + \bar{a} = 1$$

9. Absorption

$$a + a \cdot b = a$$

$$a \cdot (a + b) = a$$

10. Involution

$$\bar{\bar{a}} = a$$

11. Useful Identity


$$a + \bar{a} \cdot b = a + b = (a + \bar{a}) \cdot (a + b) = a + b$$

$$a \cdot (\bar{a} + b) = a \cdot b = a \cdot \bar{a} + a \cdot b = a \cdot b$$


MULTIPLE INPUTS

- Due to associativity, $a+b+c$ & $a \cdot b \cdot c$ require no brackets and the order does not matter.
- Using DeMorgan's Laws
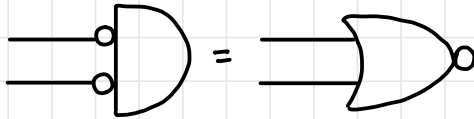
$$\bar{a} \cdot \bar{b} = \overline{a+b}$$


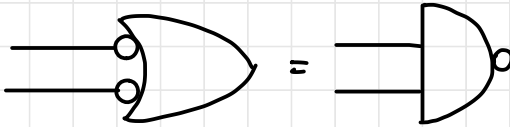
$$\bar{a+b} = \overline{\bar{a} \cdot \bar{b}}$$



logic minimisation K-MAPS

- construct Boolean formula / CLC using truth table
- using smallest two-level sum of Products formula

TERMINOLOGY

- **Literal** — Bool variable / complement (eg: \bar{z})
- **Product** — AND of two or more literals (eg: abc)
- **Minterm** — product involving all inputs to Boolean function (such that minterm product = 1)

| a | b | c | minterm | name |
|---|---|---|-------------------------|-------|
| 0 | 0 | 0 | $\bar{a}\bar{b}\bar{c}$ | m_0 |
| 0 | 0 | 1 | $\bar{a}\bar{b}c$ | m_1 |
| 0 | 1 | 0 | $\bar{a}b\bar{c}$ | m_2 |
| 0 | 1 | 1 | $\bar{a}bc$ | m_3 |
| 1 | 0 | 0 | $a\bar{b}\bar{c}$ | m_4 |
| 1 | 0 | 1 | $a\bar{b}c$ | m_5 |
| 1 | 1 | 0 | $ab\bar{c}$ | m_6 |
| 1 | 1 | 1 | abc | m_7 |

lowercase m

names
of
the
minterms

- **Sum** — OR of two or more literals (eg: $a + \bar{b} + c$)
- **Maxterm** — sum involving all inputs to Boolean function (such that maxterm sum = 0)

| a | b | c | maxterm | name |
|---|---|---|-------------------------------|-------|
| 0 | 0 | 0 | $a + b + c$ | M_0 |
| 0 | 0 | 1 | $a + b + \bar{c}$ | M_1 |
| 0 | 1 | 0 | $a + \bar{b} + c$ | M_2 |
| 0 | 1 | 1 | $a + \bar{b} + \bar{c}$ | M_3 |
| 1 | 0 | 0 | $\bar{a} + b + c$ | M_4 |
| 1 | 0 | 1 | $\bar{a} + b + \bar{c}$ | M_5 |
| 1 | 1 | 0 | $\bar{a} + \bar{b} + c$ | M_6 |
| 1 | 1 | 1 | $\bar{a} + \bar{b} + \bar{c}$ | M_7 |

uppercase M

names
of
maxterms

Sum of Products

- sum of all minterms corresponding to a 1 output

eg:

| a | b | c | y | minterm | name |
|---|---|---|---|-------------------------|-------|
| 0 | 0 | 0 | 0 | $\bar{a}\bar{b}\bar{c}$ | m_0 |
| 0 | 0 | 1 | 0 | $\bar{a}\bar{b}c$ | m_1 |
| 0 | 1 | 0 | 0 | $\bar{a}b\bar{c}$ | m_2 |
| 0 | 1 | 1 | 1 | $\bar{a}bc$ | m_3 |
| 1 | 0 | 0 | 1 | $a\bar{b}\bar{c}$ | m_4 |
| 1 | 0 | 1 | 0 | $a\bar{b}c$ | m_5 |
| 1 | 1 | 0 | 1 | $ab\bar{c}$ | m_6 |
| 1 | 1 | 1 | 1 | abc | m_7 |

- SOP form Boolean formula:

$$y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$$

$$y = m_3 + m_4 + m_6 + m_7$$

- sigma (Σ) notation

$$y = \Sigma(m_3, m_4, m_6, m_7)$$

$$y = \Sigma(3, 4, 6, 7)$$

- Boolean function f

$$y = f(a, b, c) = \Sigma(m_3, m_4, m_6, m_7)$$

- Can use 4 3-input AND gates and 1 4-input OR gate to construct CLC

Product of Sums

- product of all maxterms corresponding to a 0 output

• eg:

| a | b | c | y | maxterm | name |
|---|---|---|---|-------------------------------|-------|
| 0 | 0 | 0 | 0 | $a + b + c$ | M_0 |
| 0 | 0 | 1 | 0 | $a + b + \bar{c}$ | M_1 |
| 0 | 1 | 0 | 0 | $a + \bar{b} + c$ | M_2 |
| 0 | 1 | 1 | 1 | $a + \bar{b} + \bar{c}$ | M_3 |
| 1 | 0 | 0 | 1 | $\bar{a} + b + c$ | M_4 |
| 1 | 0 | 1 | 0 | $\bar{a} + b + \bar{c}$ | M_5 |
| 1 | 1 | 0 | 1 | $\bar{a} + \bar{b} + c$ | M_6 |
| 1 | 1 | 1 | 1 | $\bar{a} + \bar{b} + \bar{c}$ | M_7 |

- POS from Boolean formula

$$y = (a + b + c) \cdot (a + b + \bar{c}) \cdot (a + \bar{b} + c) \cdot (\bar{a} + b + \bar{c})$$

$$y = M_0 M_1 M_2 M_5$$

- Pi (Π) notation

$$y = \Pi(M_0, M_1, M_2, M_5)$$

$$y = \Pi(0, 1, 2, 5)$$

- Boolean function f

$$y = f(a, b, c) = \Pi(0, 1, 2, 5)$$

Logic Minimisation using Identities

- Consider $y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$
- Minimise using identities

$$\begin{aligned}y &= \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc \\ &= bc(a + \bar{a}) + a\bar{c}(b + \bar{b}) \\ &= bc + a\bar{c}\end{aligned}$$

Q: Prove that $ab + bc + a\bar{c} = bc + a\bar{c}$

$$\begin{aligned}ab + bc + a\bar{c} &= ab(c + \bar{c}) + bc + a\bar{c} \\ &= abc + ab\bar{c} + bc + a\bar{c} \\ &= bc(a + 1) + a\bar{c}(b + 1) \\ &= bc + a\bar{c}\end{aligned}$$

$$\begin{aligned}&= ab + \bar{a}bc + a\bar{b}\bar{c} \\ &= a(b + \bar{b}\bar{c}) + \bar{a}bc \\ &= a(b + \bar{c}) + \bar{a}bc \\ &= ab + a\bar{c} + \bar{a}bc \\ &= b(a + \bar{a}\bar{c}) + a\bar{c} \\ &= b(a + \bar{c}) + a\bar{c} \\ &= bc + a\bar{c} + ab\end{aligned}$$

Q: Minimise $(a+b+c)(a+b+\bar{c})(a+\bar{b}+c)(\bar{a}+b+\bar{c})$

$$\begin{aligned}&[(a+b) + (a+b)\bar{c} + (a+b)c] (a+\bar{b}+c) (\bar{a}+b+\bar{c}) \\ &= (a+b) (a + ab + a\bar{c} + \bar{b}\bar{a} + \bar{b}b + \bar{b}\bar{c} + c\bar{a} + cb + c) \\ &= (a+b) (ab + a\bar{c} + \bar{a}\bar{b} + \bar{b}\bar{c} + (\bar{a} + bc)) \\ &= ab + a\bar{c} + a\bar{b}\bar{c} + abc + ab + ab\bar{c} + \bar{a}bc + bc \\ &= ab(1+c) + a\bar{c}(1+\bar{b}) + ab\bar{c} + bc(1+\bar{a}) \\ &= ab + a\bar{c} + bc + ab\bar{c} \\ &= ab + a\bar{c} + bc \\ &= abc + ab\bar{c} + a\bar{c} + bc \\ &= bc + a\bar{c}\end{aligned}$$

K-Maps

- Named after Maurice Karnaugh
- Minterms that differ in one literal must be adjacent

IMPLICANTS

- K-Map area composed of squares containing 1s
- Area is square/rectangular (wraparound allowed)
- No. of squares in area is power of 2
- Each implicant \rightarrow product of literals

Prime Implicants

- Implicant with largest no. of squares obeying the rules

Essential prime Implicant

- Prime implicant containing square not in any other prime implicant

- K map method: includes all prime implicants such that each 1 square is covered and formula is minimal.
- For this TT

| a | b | c | y | minterm |
|---|---|---|---|---------------------------|
| 0 | 0 | 0 | 0 | $\bar{a}\bar{b}\bar{c}$ 0 |
| 0 | 0 | 1 | 0 | $\bar{a}\bar{b}c$ 1 |
| 0 | 1 | 0 | 0 | $\bar{a}b\bar{c}$ 2 |
| 0 | 1 | 1 | 1 | $\bar{a}bc$ 3 |
| 1 | 0 | 0 | 1 | $a\bar{b}\bar{c}$ 4 |
| 1 | 0 | 1 | 0 | $a\bar{b}c$ 5 |
| 1 | 1 | 0 | 1 | abc 6 |
| 1 | 1 | 1 | 1 | abc 7 |

| a \ bc | 00 | 01 | 11 | 10 |
|--------|---------------------------|---------------------|---------------------|---------------|
| 0 | 0 $\bar{a}\bar{b}\bar{c}$ | 1 $\bar{a}\bar{b}c$ | 3 $\bar{a}b\bar{c}$ | 2 $\bar{a}bc$ |
| 1 | 4 $a\bar{b}\bar{c}$ | 5 $a\bar{b}c$ | 7 abc | 6 $ab\bar{c}$ |

Example 1

1. Prime implicants — green
2. Essential — blue
3. Required — red

| | | | | | |
|---|----|----------------|----------------|----------------|----------------|
| | bc | 00 | 01 | 11 | 10 |
| a | | 00 | 01 | 11 | 10 |
| 0 | | 0 ₀ | 0 ₁ | 1 ₃ | 0 ₂ |
| 1 | | 1 ₄ | 0 ₅ | 1 ₇ | 1 ₆ |

| | | | | | |
|---|----|----------------|----------------|----------------|----------------|
| | bc | 00 | 01 | 11 | 10 |
| a | | 00 | 01 | 11 | 10 |
| 0 | | 0 ₀ | 0 ₁ | 1 ₃ | 0 ₂ |
| 1 | | 1 ₄ | 0 ₅ | 1 ₇ | 1 ₆ |

| | | | | | |
|-----------|----|------------------|----------------|----------------|----------------|
| | bc | $\bar{b}\bar{c}$ | $\bar{b}c$ | bc | $b\bar{c}$ |
| a | | 00 | 01 | 11 | 10 |
| \bar{a} | 0 | 0 ₀ | 0 ₁ | 1 ₃ | 0 ₂ |
| a | 1 | 1 ₄ | 0 ₅ | 1 ₇ | 1 ₆ |

(3 & 4 only covered by these 2)

SOP: $a\bar{c} + bc$ (unchanging terms)

Example 2

| | | | | | |
|---|----|----------------|----------------|----------------|----------------|
| | bc | 00 | 01 | 11 | 10 |
| a | | 00 | 01 | 11 | 10 |
| 0 | | 0 ₀ | 1 ₁ | 1 ₃ | 0 ₂ |
| 1 | | 1 ₄ | 1 ₅ | 1 ₇ | 1 ₆ |

| | | | | | |
|---|----|----------------|----------------|----------------|----------------|
| | bc | 00 | 01 | 11 | 10 |
| a | | 00 | 01 | 11 | 10 |
| 0 | | 0 ₀ | 1 ₁ | 1 ₃ | 0 ₂ |
| 1 | | 1 ₄ | 1 ₅ | 1 ₇ | 1 ₆ |

| a \ bc | $\bar{b}\bar{c}$ | $\bar{b}c$ | $b\bar{c}$ | bc |
|-----------|------------------|----------------|----------------|----------------|
| a | | | | |
| \bar{a} | 0 ₀ | 1 ₁ | 1 ₃ | 0 ₂ |
| a | 1 ₄ | 1 ₅ | 1 ₇ | 1 ₆ |

(1,3 & 4,6)

$$\text{SOP: } c + a = f(a,b,c)$$

Example 3

| a \ bc | 00 | 01 | 11 | 10 |
|--------|----------------|----------------|----------------|----------------|
| a | | | | |
| 0 | 0 ₀ | 1 ₁ | 0 ₃ | 1 ₂ |
| 1 | 0 ₄ | 1 ₅ | 1 ₇ | 1 ₆ |

| a \ bc | 00 | 01 | 11 | 10 |
|--------|----------------|----------------|----------------|----------------|
| a | | | | |
| 0 | 0 ₀ | 1 ₁ | 0 ₃ | 1 ₂ |
| 1 | 0 ₄ | 1 ₅ | 1 ₇ | 1 ₆ |

| a \ bc | $\bar{b}\bar{c}$ | $\bar{b}c$ | $b\bar{c}$ | bc |
|-----------|------------------|----------------|----------------|----------------|
| a | | | | |
| \bar{a} | 0 ₀ | 1 ₁ | 0 ₃ | 1 ₂ |
| a | 0 ₄ | 1 ₅ | 1 ₇ | 1 ₆ |

| a \ bc | $\bar{b}\bar{c}$ | $\bar{b}c$ | $b\bar{c}$ | bc |
|-----------|------------------|----------------|----------------|----------------|
| a | | | | |
| \bar{a} | 0 ₀ | 1 ₁ | 0 ₃ | 1 ₂ |
| a | 0 ₄ | 1 ₅ | 1 ₇ | 1 ₆ |

$$\text{SOP} = \bar{b}c + \bar{b}\bar{c} + ca$$

$$\text{SOP} = \bar{b}c + \bar{b}\bar{c} + ba$$

(no unique solution)

Example 4

| | | cd | $\bar{c}\bar{d}$ | $\bar{c}d$ | $c\bar{d}$ |
|----|---------------------|----------------|------------------|-----------------|-----------------|
| | | 00 | 01 | 11 | 10 |
| ab | $\bar{a}\bar{b}$ 00 | 1 ₀ | | | 1 ₂ |
| | $\bar{a}b$ 01 | | 1 ₄ | 1 ₅ | 1 ₆ |
| ab | $a\bar{b}$ 11 | | 1 ₁₂ | 1 ₁₃ | |
| | ab 10 | 1 ₈ | | | 1 ₁₀ |

| | | cd | $\bar{c}\bar{d}$ | $\bar{c}d$ | $c\bar{d}$ |
|----|---------------------|----------------|------------------|-----------------|-----------------|
| | | 00 | 01 | 11 | 10 |
| ab | $\bar{a}\bar{b}$ 00 | 1 ₀ | | | 1 ₂ |
| | $\bar{a}b$ 01 | | 1 ₄ | 1 ₅ | 1 ₆ |
| ab | $a\bar{b}$ 11 | | 1 ₁₂ | 1 ₁₃ | |
| | ab 10 | 1 ₈ | | | 1 ₁₀ |

| | | cd | $\bar{c}\bar{d}$ | $\bar{c}d$ | $c\bar{d}$ |
|----|---------------------|----------------|------------------|-----------------|-----------------|
| | | 00 | 01 | 11 | 10 |
| ab | $\bar{a}\bar{b}$ 00 | 1 ₀ | | | 1 ₂ |
| | $\bar{a}b$ 01 | | 1 ₄ | 1 ₅ | 1 ₆ |
| ab | $a\bar{b}$ 11 | | 1 ₁₂ | 1 ₁₃ | |
| | ab 10 | 1 ₈ | | | 1 ₁₀ |

$$\text{SOP} = db + \bar{a}\bar{b}$$

Example 5

| a | b | y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

| | | \bar{b} | b |
|---|-------------|----------------|----------------|
| | | 0 | 1 |
| a | \bar{a} 0 | 1 ₀ | 0 ₁ |
| | a 1 | 1 ₂ | 1 ₃ |

$$\text{SOP} = \bar{b} + a$$

DON'T CARES

- If we know for a fact that certain input combinations cannot occur in a logic gate, we place a don't care
- The logic circuit will never receive that input combination, so we don't care if it's a 0 or a 1

Example 6 green - required (? = X)

| | | | | | |
|---|--|----------------|----------------|----------------|----------------|
| | | bc | | | |
| a | | 00 | 01 | 11 | 10 |
| 0 | | 1 ₀ | 1 ₁ | 0 ₃ | 0 ₂ |
| 1 | | 1 ₄ | 1 ₅ | X ₇ | 1 ₆ |

Do for both 0 and 1

| | | | | | | |
|-----------|---|----------------|------------------|----------------|----------------|------|
| | | bc | $\bar{b}\bar{c}$ | $\bar{b}c$ | $b\bar{c}$ | bc |
| a | | 00 | 01 | 11 | 10 | |
| \bar{a} | 0 | 1 ₀ | 1 ₁ | 0 ₃ | 0 ₂ | |
| a | 1 | 1 ₄ | 1 ₅ | 0 ₇ | 1 ₆ | |

$$SOP = y = \bar{b} + \bar{c}a$$

| | | | | | | |
|-----------|---|----------------|------------------|----------------|----------------|------|
| | | bc | $\bar{b}\bar{c}$ | $\bar{b}c$ | $b\bar{c}$ | bc |
| a | | 00 | 01 | 11 | 10 | |
| \bar{a} | 0 | 1 ₀ | 1 ₁ | 0 ₃ | 0 ₂ | |
| a | 1 | 1 ₄ | 1 ₅ | 1 ₇ | 1 ₆ | |

$$SOP = y = \bar{b} + a$$

- Whichever results in a smaller Boolean formula is used

Example 7

$$f(a,b,c,d) = \Sigma(m_3, m_4, m_5, m_7, m_9, m_{13}, m_{14}, m_{15})$$

| ab \ cd | $\bar{c}\bar{d}$ 00 | $\bar{c}d$ 01 | cd 11 | $c\bar{d}$ 10 |
|---------------------|------------------------|------------------|-----------------|------------------|
| $\bar{a}\bar{b}$ 00 | 0 ₀ | 0 ₁ | 1 ₃ | 0 ₂ |
| $\bar{a}b$ 01 | 1 ₄ | 1 ₅ | 1 ₇ | 0 ₆ |
| ab 11 | 0 ₁₂ | 1 ₁₃ | 1 ₁₅ | 1 ₁₄ |
| $a\bar{b}$ 10 | 0 ₈ | 1 ₉ | 0 ₁₁ | 0 ₁₀ |

$$y = \bar{c}\bar{a}b + cd\bar{a} + abc + \bar{c}da$$

Example 8

$$f(a,b,c,d) = \Sigma(0, 1, 2, 6, 8, 9, 10)$$

| ab \ cd | $\bar{c}\bar{d}$ 00 | $\bar{c}d$ 01 | cd 11 | $c\bar{d}$ 10 |
|---------------------|------------------------|------------------|-----------------|------------------|
| $\bar{a}\bar{b}$ 00 | 1 ₀ | 1 ₁ | 0 ₃ | 1 ₂ |
| $\bar{a}b$ 01 | 0 ₄ | 0 ₅ | 0 ₇ | 1 ₆ |
| ab 11 | 0 ₁₂ | 0 ₁₃ | 0 ₁₅ | 0 ₁₄ |
| $a\bar{b}$ 10 | 1 ₈ | 1 ₉ | 0 ₁₁ | 1 ₁₀ |

$$y = \bar{c}\bar{b} + \bar{a}c\bar{d} + \bar{b}c\bar{d}$$

Example 9

$$f(a,b,c,d) = \sum(0,2,3,5,7,8,9,10,11,13,15)$$

| ab \ cd | $\bar{c}\bar{d}$ | $\bar{c}d$ | cd | $c\bar{d}$ |
|---------------------|------------------|-----------------|-----------------|-----------------|
| $\bar{a}\bar{b}$ 00 | 1 ₀ | | 1 ₂ | 1 ₂ |
| $\bar{a}b$ 01 | | 1 ₄ | 1 ₅ | |
| ab 11 | | 1 ₁₂ | 1 ₁₃ | 1 ₁₄ |
| $a\bar{b}$ 10 | 1 ₈ | 1 ₉ | 1 ₁₁ | 1 ₁₀ |

$$y = bd + \bar{b}c + a\bar{b} + \bar{a}\bar{b}$$

not the only solution

Example 10

$$f(a,b,c,d) = \sum(1,3,10) + \sum_d(0,2,8,12)$$

don't care

| ab \ cd | $\bar{c}\bar{d}$ | $\bar{c}d$ | cd | $c\bar{d}$ |
|---------------------|------------------|-----------------|-----------------|-----------------|
| $\bar{a}\bar{b}$ 00 | X ₀ | 1 ₁ | 1 ₃ | X ₂ |
| $\bar{a}b$ 01 | 0 ₄ | 0 ₅ | 0 ₇ | 0 ₆ |
| ab 11 | X ₁₂ | 0 ₁₃ | 0 ₁₅ | 0 ₁₄ |
| $a\bar{b}$ 10 | X ₈ | 0 ₉ | 0 ₁₁ | 1 ₁₀ |

$$y = \bar{a}\bar{b} + \bar{a}b$$

Example 11

$$f(w,x,y,z) = \sum(1,3,7,11,15) + \sum_d(0,2,5)$$

| wx \ yz | $\bar{y}\bar{z}$ 00 | $\bar{y}z$ 01 | $y\bar{z}$ 11 | yz 10 |
|---------------------|------------------------|------------------|------------------|----------------|
| $\bar{w}\bar{z}$ 00 | X ₀ | 1 ₁ | 1 ₃ | X ₂ |
| $\bar{w}z$ 01 | | X ₅ | 1 ₇ | |
| wx 11 | | | 1 ₁₁ | |
| w \bar{z} 10 | | | 1 ₁₅ | |

$$SOP = \bar{w}\bar{z} + yz$$

BINARY NUMBERS

1) Unsigned
2) Signed] representation

UNSIGNED

5 - 101
4 - 100

$$m = \sum_{i=0}^{n-1} x_i \times 2^i$$

n = no. of digits
 x_i = digit

SIGNED

MSB indicates sign

MSB 1 \rightarrow -ve

MSB 0 \rightarrow +ve

Represent Positive No.s

+5 \rightarrow 0101

+6 \rightarrow 0110

Represent Negative No.s (three ways)

1. Simple Sign Magnitude

+5 \rightarrow 0101

-5 \rightarrow 1101

2. 1's complement

$$\begin{aligned} +5 &\longrightarrow 0101 \\ \text{1's complement} &\longrightarrow 1010 \\ -5 &\longrightarrow 1010 \end{aligned}$$

invert all 0's and 1's

problem: $+0$ and -0 are different

$$\begin{aligned} +0 &\longrightarrow 0000 \\ -0 &\longrightarrow 1111 \end{aligned}$$

3. 2's Complement

- we do not use sign magnitude or 1's complement forms
- 1's comp + 1

$$\begin{aligned} +5 &\longrightarrow 0101 \\ \text{1's comp} &\longrightarrow 1010 \\ -5 &\longrightarrow 1011 \longrightarrow \text{2's complement} \end{aligned}$$

- advantage: 0 is universal

$$\begin{aligned} +0 &\longrightarrow 0000 \\ \text{1's comp} &\longrightarrow 1111 \\ -0 &\longrightarrow 0000 \quad (\text{overflow}) \end{aligned}$$

- 2's complement of 2's complement is the original no.
- used in comps

• Eg: $+5 \rightarrow 0101$
 \downarrow 2's complement

$-5 \rightarrow 1011$
 \downarrow 2's complement

$+5 \rightarrow 0101$

Intuition :

$-5 \rightarrow 1011 \rightarrow +1$
 $-4 \rightarrow 1100 \rightarrow +1$

\therefore can add 2's comp to +ve no. for subtraction

• for an n-bit signed no, 2^{n-1} no.s for 0 & +ve,
 2^{n-1} for -ve

| | | | |
|------|---|------|----|
| 0000 | 0 | 1000 | -8 |
| 0001 | 1 | 1001 | -7 |
| 0010 | 2 | 1010 | -6 |
| 0011 | 3 | 1011 | -5 |
| 0100 | 4 | 1100 | -4 |
| 0101 | 5 | 1101 | -3 |
| 0110 | 6 | 1110 | -2 |
| 0111 | 7 | 1111 | -1 |

adding and subtracting binary numbers

ADDITION

- binary addition

$$5 + 3$$

$$\begin{array}{r} 111 \\ 0101 \\ + 0011 \\ \hline 1000 \end{array} = 8$$

SUBTRACTION

- to do $a - b$ do $a + (-b)$ or $a + 2$'s complement of b
- note: signed vs unsigned addition
- $3 - 5 = -5 + 3$

$$\begin{array}{r} 1011 \\ + 0011 \\ \hline 1110 \end{array}$$

→ find 2's comp

$$0001 + 1 = 0010$$

$$\therefore \text{res} = -2$$

Example 12

- Add 0111 and 1011 deal with overflow
 \hookrightarrow signed
 \hookrightarrow unsigned

unsigned

$$\begin{array}{r} 0111 \\ + 1011 \\ \hline 10010 = 2 \\ \text{overflow is} \end{array}$$

signed

$$\begin{array}{r} 0111 \\ + 1011 \\ \hline 10010 = 2 \\ \text{no overflow?} \end{array}$$

There are 2 4-bit no.s whose 2's complement does not reverse the sign

1. $0000 \rightarrow 0$



2's comp: $1111 + 1 = 10000$ ← overflow

2. $1000 \rightarrow -8$

2's comp: $0111 + 1 \rightarrow 1000 \rightarrow -8$

LOGIC CIRCUITS FOR ADDITION

structure of logic circuits

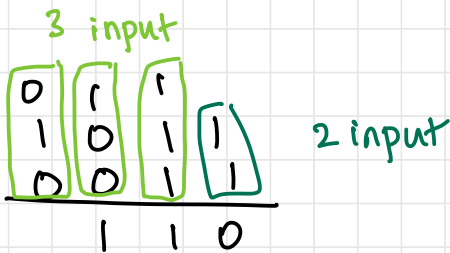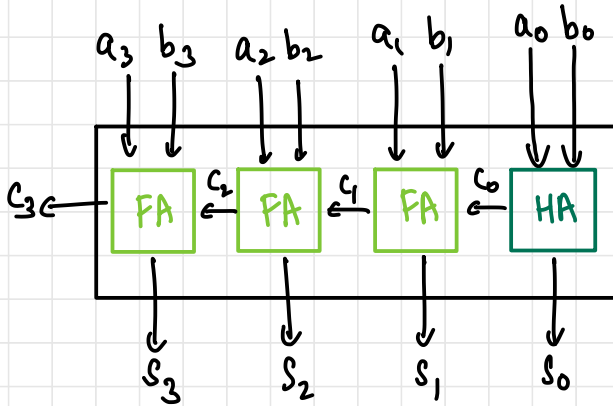

- LSB: 2-input adder — half adder (HA)
- all other bits: 3-input adder — full adder (FA)

HALF ADDER

Truth Table


| inputs | | outputs | |
|--------|---|---------|---|
| a | b | s | c |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

- SOP formulas (minterms)

$$s = \bar{a}b + a\bar{b} \quad (\text{XOR function})$$

$$s = a \oplus b$$

$$c = ab \quad (\text{AND function})$$

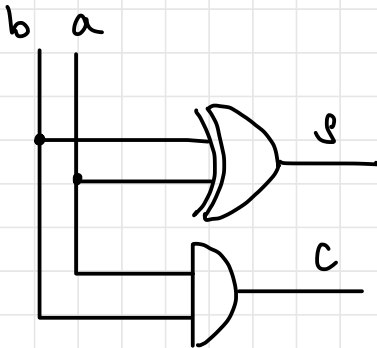

FULL ADDER

| a | b | c | s | C _{out} |
|---|---|---|---|------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |


- SOP formulas

$$s = \bar{a}bc + a\bar{b}c + ab\bar{c} + abc$$

$$s = a \oplus b \oplus c$$

$$c_{out} = \bar{a}bc + a\bar{b}c + ab\bar{c} + abc$$
$$= bc(a + \bar{a}) + ac(b + \bar{b}) + ab(c + \bar{c})$$

$$c_{out} = ab + bc + ac$$

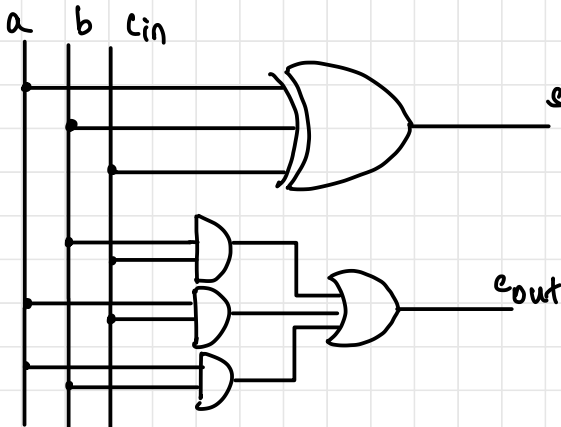


Example 13 - HW

Perform binary subtraction (not addition) and draw logic circuits

$$\begin{array}{r} 0 \quad 1 \\ \cancel{1} \quad \cancel{0} \quad 0 \quad 1 \\ - \quad 0 \quad 0 \quad 1 \quad 1 \\ \hline 0 \quad 1 \quad 1 \quad 0 \end{array}$$

$$\begin{array}{r} 9 \\ - 3 \\ \hline 6 \end{array}$$
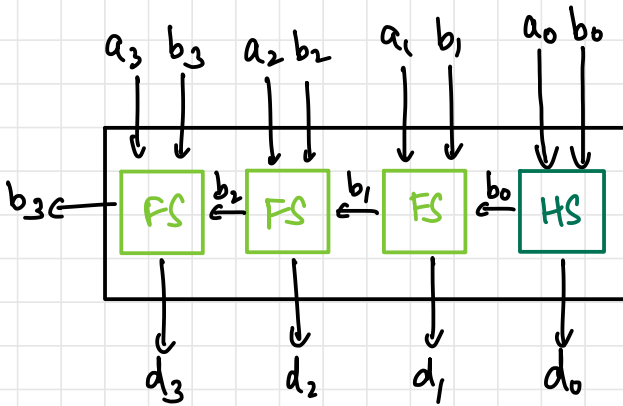
$$\begin{array}{r} 1 \quad 1 \\ 1 \quad 0 \quad 0 \quad 1 \\ - 0 \quad 0 \quad 1 \quad 1 \\ \hline 0 \quad 1 \quad 1 \quad 0 \end{array}$$



$$6 - 3 = 3$$

$$\begin{array}{r} 1 \quad 1 \\ 0 \quad 1 \quad 1 \quad 0 \\ - 0 \quad 0 \quad 1 \quad 1 \\ \hline 0 \quad 0 \quad 1 \quad 1 \end{array}$$

$$5 - 2 = 3$$

$$\begin{array}{r} 1 \\ 0 \quad 1 \quad 0 \quad 1 \\ - 0 \quad 0 \quad 1 \quad 0 \\ \hline 0 \quad 0 \quad 1 \quad 1 \end{array}$$

$$a - b_{in} - b$$


HALF SUBTRACTOR

| a | b | d | b _{out} |
|---|---|---|------------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

SOP Formulas

$$d = \bar{a}b + a\bar{b} = a \oplus b$$

$$b_{out} = \bar{a}b$$

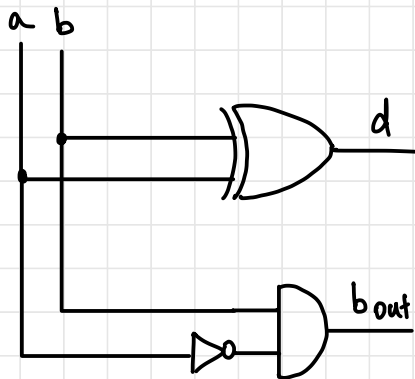

FULL SUBTRACTOR

$$\begin{aligned} a - b - b_{in} &\longrightarrow \\ &= -1 (+2) \\ &= 1 \end{aligned}$$

$$\begin{aligned} a - b - b_{in} &\longrightarrow \\ &= -1 (+2) \\ &= 1 \end{aligned}$$

| a | b | $c - b_{in}$ | d | b_{out} |
|---|---|--------------|---|-----------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

$$a - b_{in} - b$$

if $a < b + b_{in}$

2 is added to
current digit


$$d = a \oplus b \oplus c$$

$$\begin{aligned} b_{out} &= \bar{a}\bar{b}c + \bar{a}b\bar{c} + \bar{a}bc + abc \\ &= bc(a + \bar{a}) + \bar{a}b(c + \bar{c}) + \bar{a}c(b + \bar{b}) \end{aligned}$$

$$b_{out} = bc + \bar{a}b + \bar{a}c$$


INCREMENT LOGIC CIRCUIT

- $b + 1$


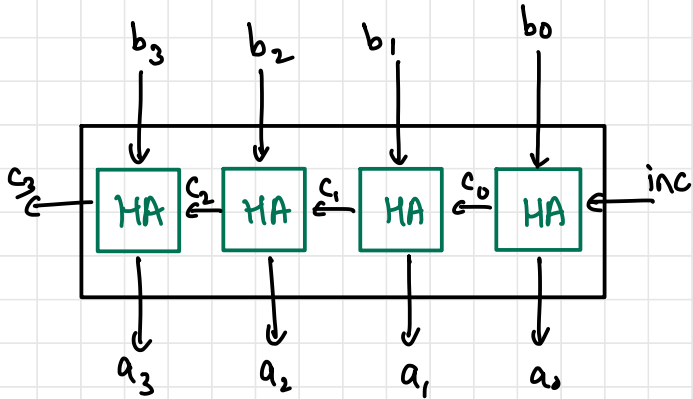


TWO'S COMPLEMENT

- b inverted + 1

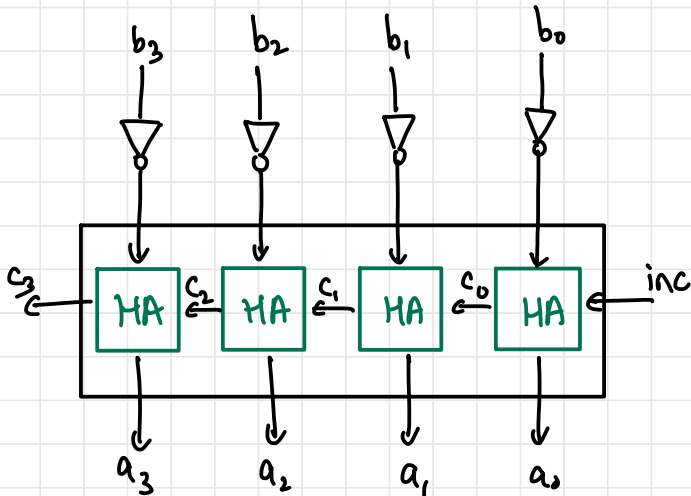


TWO'S COMPLEMENT SUBTRACTOR

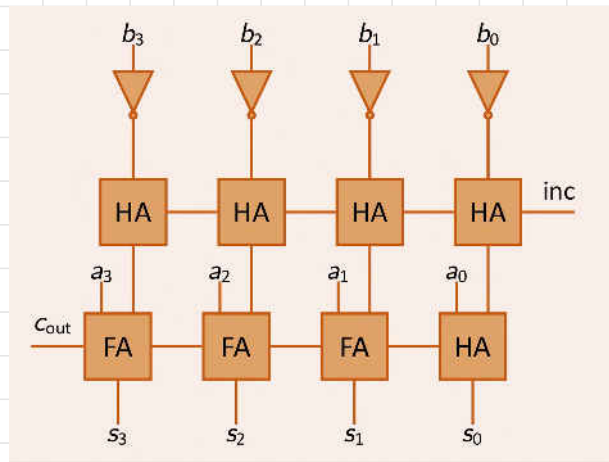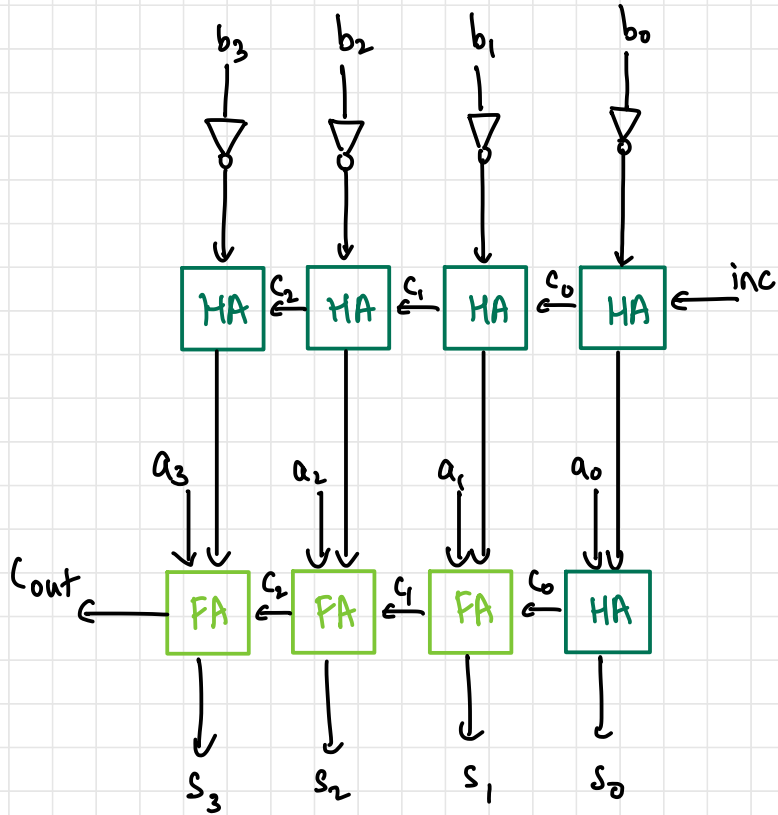

TWO'S COMPLEMENT ADDER/SUBTRACTOR

XOR as Controlled Inverter

| inv | a | y |
|-----|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

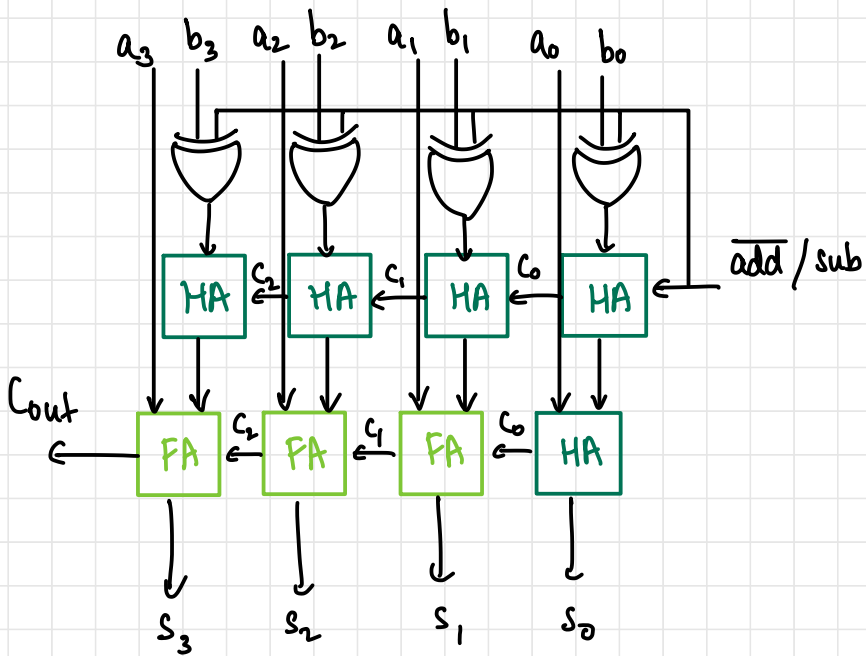


INCREMENTOR WITHOUT INC INPUT


first incrementor

| a | s | c |
|---|---|---|
| 0 | 1 | 0 |
| 1 | 0 | 1 |


$$s = \bar{a}$$
$$c = a$$

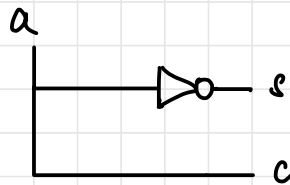

half incrementor
HA

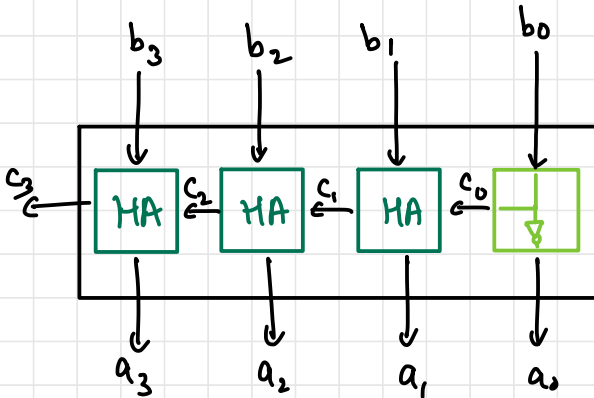

OR

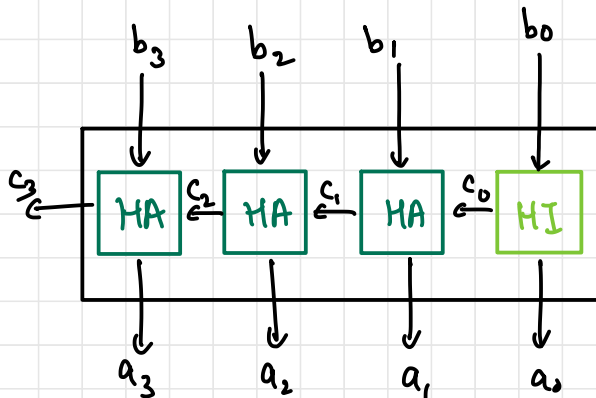

DECREMENTOR

• $b - 1 = b + (-1)$

TWO'S COMPLEMENT DECREMENTOR

• $-1 = (1111)$

$$\begin{array}{r} 11 \\ 0110 \quad 6 \\ + 1111 \quad (-1) \\ \hline \end{array}$$

→ 00101 5


no overflow

$$\begin{array}{r} 1 \\ 0110 \quad 6 \\ - 0001 \quad (-1) \\ \hline 0101 \quad 5 \end{array}$$

Half 2's Complement Decrementor

| a | s | c |
|---|---|---|
| 0 | 1 | 1 |
| 1 | 0 | 0 |
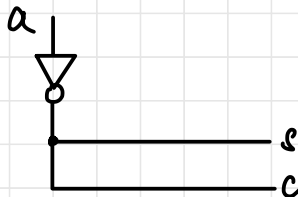
$$\begin{aligned} s &= \bar{a} \\ c &= \bar{a} \end{aligned}$$





Full 2's Complement Decrementor

| a | $C_{in}=b$ | S | C_{out} |
|-----|------------|-----|-----------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

$$S = \bar{a}b + a\bar{b} \quad (\text{XOR})$$

$$C = \bar{a}b$$


Full decrementor
FD

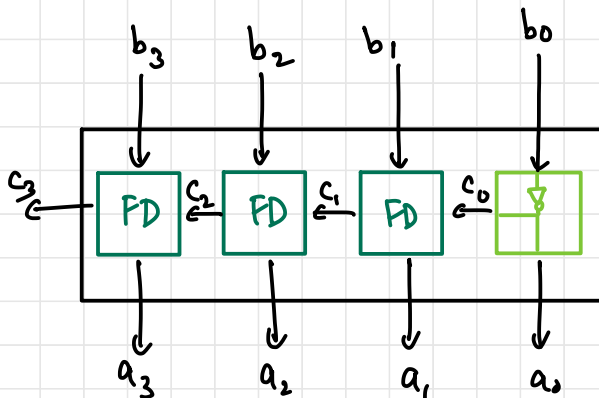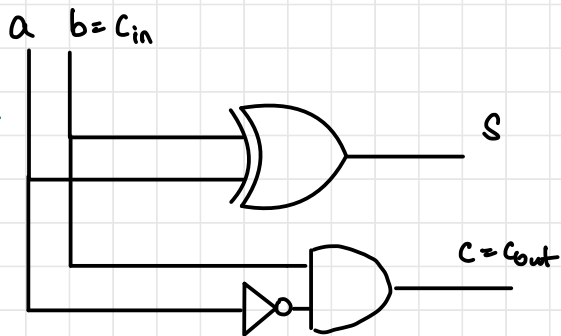

Overflow

- Logic circuits have fixed bit widths
- Eg: 64 bit processor
- if result of an operation does not fit within the bit width

SIMPLE ADDITION

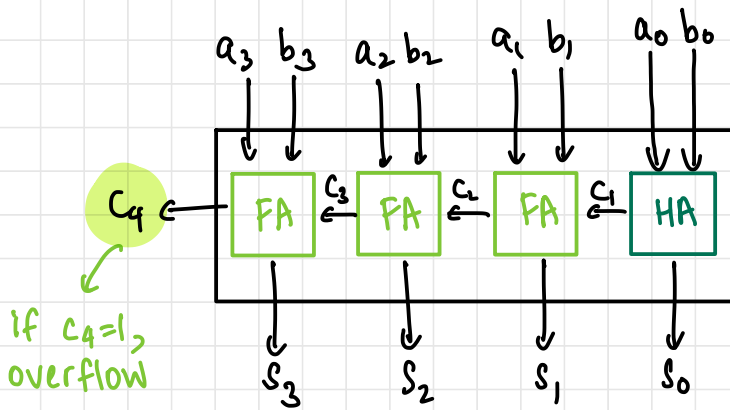

TWO'S COMPLEMENT ADDITION

- three cases

Case I - no overflow

one +ve, one -ve
a +ve, b -ve

case i

$$|a| > |b|$$

result: +ve

case ii

$$|b| > |a|$$

result: -ve

case iii

$$|a| = |b|$$

result: 0

Case II - overflow occurs

both +ve

→ MSB is 1 (C_{msb} is 1) ←

should not happen
in 2's Comp +ve

→ C_{msb} is 1 and C_{msb+1} is 0


Case III - overflow occurs

both -ve

→ msb is 0 (C_{msb} is 0)

→ C_{msb} is 0 and C_{msb+1} is 1
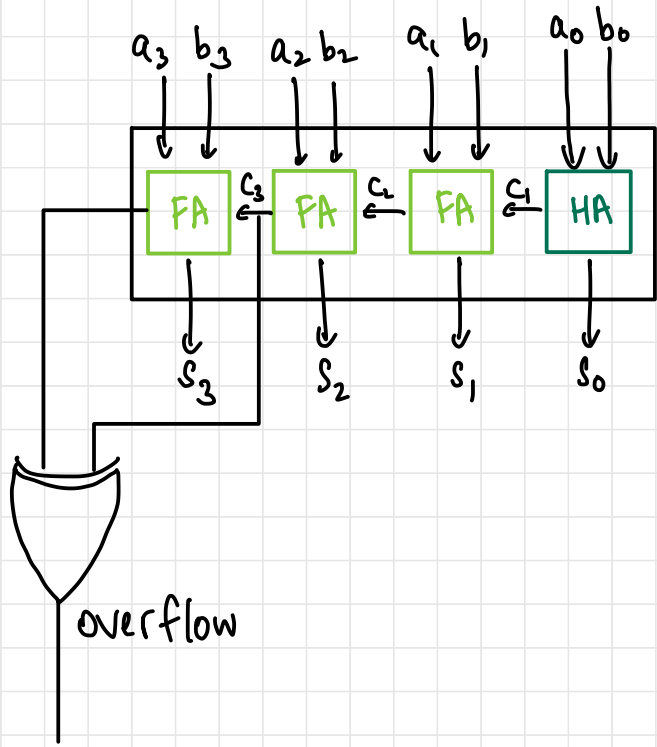
$$\text{overflow} = C_{msb} \oplus C_{msb+1}$$



Question

Design combinational circuit for 3 I/P & 1 O/P.
The O/P is 1 when the binary value of the input is less than 3. The O/P is 0 otherwise

| a | b | c | y |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

$$y = \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + \bar{a}b\bar{c}$$

$$y = \bar{a}\bar{b} + \bar{a}b\bar{c} + \bar{a}\bar{b}c$$
$$= \bar{a}\bar{b} + \bar{a}\bar{c}$$

$$y = \bar{a}\bar{b} + \bar{a}\bar{c}$$

Question

Design combinational circuit for 3 I/P & 1 O/P.
The O/P is 1 when the binary value of the input is even. The O/P is 0 otherwise

| a | b | c | y |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

| | bc | | | |
|---|----------------|----------------|----------------|----------------|
| a | 00 | 01 | 11 | 10 |
| 0 | 1 ₀ | 0 ₁ | 0 ₃ | 1 ₂ |
| 1 | 1 ₄ | 0 ₅ | 0 ₇ | 1 ₆ |

$$y = \bar{c}$$

Question

Design combinational circuit for 3 I/P x, y, z and 3 O/Ps a, b, c . When I/P is 0, 1, 2 or 3, O/P is one greater than I/P. When I/P is 4, 5, 7 or 7, O/P is 2 less than I/P.

| x | y | z | a | b | c |
|-----|-----|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 |

a

| $x \backslash yz$ | $\bar{y}\bar{z}$ 00 | $\bar{y}z$ 01 | $y\bar{z}$ 11 | yz 10 |
|-------------------|------------------------|------------------|------------------|----------------|
| \bar{x} 0 | 0 ₀ | 0 ₁ | 1 ₃ | 0 ₂ |
| x 1 | 0 ₄ | 0 ₅ | 1 ₇ | 1 ₆ |

$$a = yz + xy$$

b

| $x \backslash yz$ | $\bar{y}\bar{z}$ 00 | $\bar{y}z$ 01 | $y\bar{z}$ 11 | yz 10 |
|-------------------|------------------------|------------------|------------------|----------------|
| \bar{x} 0 | 0 ₀ | 1 ₁ | 0 ₃ | 1 ₂ |
| x 1 | 1 ₄ | 1 ₅ | 0 ₇ | 0 ₆ |

$$b = \bar{x}y\bar{z} + \bar{y}z + x\bar{y}$$


c

| $x \backslash yz$ | $\bar{y}\bar{z}$ 00 | $\bar{y}z$ 01 | $y\bar{z}$ 11 | yz 10 |
|-------------------|------------------------|------------------|------------------|----------------|
| \bar{x} 0 | 1 ₀ | 0 ₁ | 0 ₃ | 1 ₂ |
| x 1 | 0 ₄ | 1 ₅ | 1 ₇ | 0 ₆ |

$$c = xz + \bar{x}\bar{z}$$

Question

Logic circuit for 7-segment display

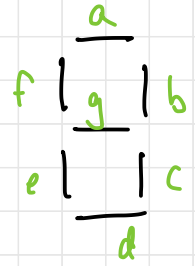

| a | b | c | d | a | b | c | d | e | f | g | |
|---|---|---|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 |
| 2 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 2 |
| 3 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 3 |
| 4 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 4 |
| 5 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 5 |
| 6 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 6 |
| 7 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 7 |
| 8 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 8 |
| 9 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 9 |